

- This is a closed book exam.
- The exam has 5 questions in two pages, answer all of them.
- Good Luck!

1. a) For the network in Figure 1, determine the level of capacitance that will ensure maximum power to the load if the range of capacitance is limited to 1 nF to 10 nF.
- b) Using the results of part (a), determine the value of R_L that will ensure maximum power to the load.
- c) Using the results of parts (a) and (b), determine the maximum power to the load. [10 marks]


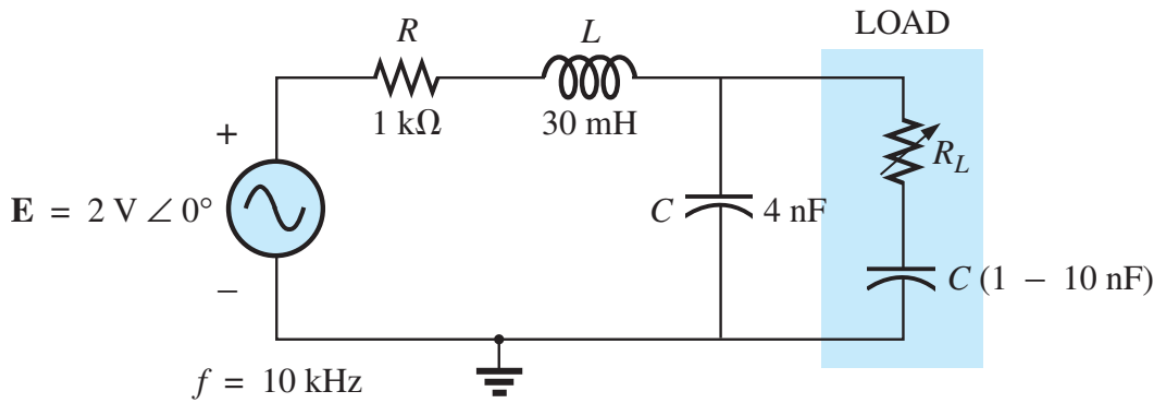


Figure 1

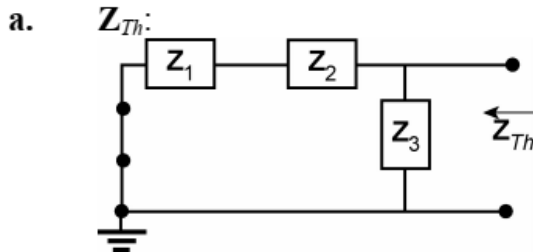

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(10 \text{ kHz})(4 \text{ nF})}$$

$$\cong 3978.87 \Omega$$

$$X_L = 2\pi fL = 2\pi(10 \text{ kHz})(30 \text{ mH})$$

$$\cong 1884.96 \Omega$$

$$Z_1 = 1 \text{ k}\Omega \angle 0^\circ, Z_2 = 1884.96 \Omega \angle 90^\circ$$

$$Z_3 = 3978.87 \Omega \angle -90^\circ$$

$$Z_{Th} = (Z_1 + Z_2) \parallel Z_3 = (1 \text{ k}\Omega + j1884.96 \Omega) \parallel 3978.87 \Omega \angle -90^\circ$$

$$= 2133.79 \Omega \angle 62.05^\circ \parallel 3978.87 \Omega \angle -90^\circ$$

$$= 3658.65 \Omega \angle 36.52^\circ$$

$$\therefore Z_L = 3658.65 \Omega \angle -36.52^\circ = 2940.27 \Omega - j2177.27 \Omega$$

$$C = \frac{1}{2\pi fX_C} = \frac{1}{2\pi(10 \text{ kHz})(2177.27 \Omega)} = 7.31 \text{ nF}$$

b. $R_L = R_{Th} = 2940.27 \Omega$

c. $E_{Th} = \frac{Z_3(E)}{Z_3 + Z_1 + Z_2} = \frac{(3978.87 \Omega \angle -90^\circ)(2 \text{ V} \angle 0^\circ)}{1 \text{ k}\Omega + j1884.96 \Omega - j3978.87 \Omega} = 3.43 \text{ V} \angle -25.53^\circ$

$$P_{\max} = E_{Th}^2 / 4R_{Th} = (3.43 \text{ V})^2 / 4(2940.27 \Omega) = 1 \text{ mW}$$

2. For the circuit shown in Figure 2, Find the Norton's equivalent as “seen” by the load resistor R_L . [10 marks]

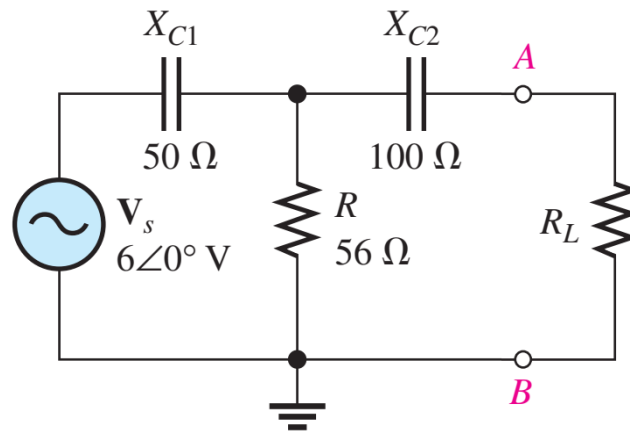


Figure 3

I_n is the current through the short and is calculated as follows. First, the total impedance viewed from the source is

$$\begin{aligned} \mathbf{Z} &= \mathbf{X}_{C1} + \frac{\mathbf{R}\mathbf{X}_{C2}}{\mathbf{R} + \mathbf{X}_{C2}} = 50 \angle -90^\circ \Omega + \frac{(56 \angle 0^\circ \Omega)(100 \angle -90^\circ \Omega)}{56 \Omega - j100 \Omega} \\ &= 50 \angle -90^\circ \Omega + 48.9 \angle -29.3^\circ \Omega \\ &= -j50 \Omega + 42.6 \Omega - j23.9 \Omega = 42.6 \Omega - j73.9 \Omega \end{aligned}$$

Converting to polar form yields

$$\mathbf{Z} = 85.3 \angle -60.0^\circ \Omega$$

Next, the total current from the source is

$$\mathbf{I}_s = \frac{\mathbf{V}_s}{\mathbf{Z}} = \frac{6 \angle 0^\circ \text{ V}}{85.3 \angle -60.0^\circ \Omega} = 70.3 \angle 60.0^\circ \text{ mA}$$

Finally, apply the current-divider formula to get \mathbf{I}_n (the current through the short between terminals A and B).

$$\mathbf{I}_n = \left(\frac{\mathbf{R}}{\mathbf{R} + \mathbf{X}_{C2}} \right) \mathbf{I}_s = \left(\frac{56 \angle 0^\circ \Omega}{56 \Omega - j100 \Omega} \right) 70.3 \angle 60.0^\circ \text{ mA} = \mathbf{34.4 \angle 121^\circ \text{ mA}}$$

3. Determine $v_o(t)$ for the op amp circuit in Figure 3.


[10 marks]

$$2 \sin(400t) \longrightarrow 2 \angle 0^\circ, \quad \omega = 400$$

$$0.5 \mu\text{F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(400)(0.5 \times 10^{-6})} = -j5 \text{ k}\Omega$$

$$0.25 \mu\text{F} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(400)(0.25 \times 10^{-6})} = -j10 \text{ k}\Omega$$

Consider the circuit as shown below.

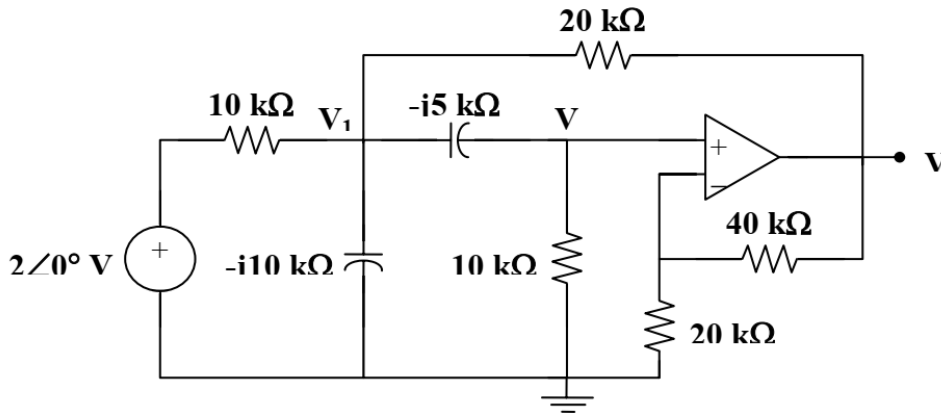

At node 1,

$$\frac{2 - V_1}{10} = \frac{V_1}{-j10} + \frac{V_1 - V_2}{-j5} + \frac{V_1 - V_o}{20}$$

$$4 = (3 + j6)V_1 - j4V_2 - V_o \quad (1)$$

At node 2,

$$\frac{V_1 - V_2}{-j5} = \frac{V_2}{10}$$

$$V_1 = (1 - j0.5)V_2 \quad (2)$$

But

$$V_2 = \frac{20}{20 + 40} V_o = \frac{1}{3} V_o \quad (3)$$

From (2) and (3),

$$V_1 = \frac{1}{3} \cdot (1 - j0.5) V_o \quad (4)$$

Substituting (3) and (4) into (1) gives

$$4 = (3 + j6) \cdot \frac{1}{3} \cdot (1 - j0.5) V_o - j\frac{4}{3} V_o - V_o = \left(1 + j\frac{1}{6}\right) V_o$$

$$V_o = \frac{24}{6 + j} = 3.945 \angle -9.46^\circ$$

Therefore,

$$v_o(t) = \underline{\underline{3.945 \sin(400t - 9.46^\circ) \text{ V}}}$$

4. Complete the following sentences:

[10 marks]

- i. For a certain load, the true power is 10 W and the reactive power is 10 VAR.
The apparent power is **14.14 VA.**
- ii. A low pass filter is a circuit that **Blocks high-frequency signals from passing through.**
- iii. An ideal operational amplifier has **zero output impedance and infinite input impedance.**
- iv. The Q factor of a coil is given by **X_L/R .**
- v. Series resonance occurs when **$X_L = X_C$.**
- vi. Increasing the number of magnetic poles in a basic generator will **increase the generator's output frequency** .
- vii. A transformer is plugged into a 120 V rms source and has a primary current of 300 mA rms. The secondary is providing 18 V rms across a $10\ \Omega$ load, the efficiency of the transformer is **90%**
- viii. The maximum output voltage of a certain low-pass filter is 15 V. The output voltage at the critical frequency is **10.60 V**
- ix. The impedance at the resonant frequency of a series RLC circuit with $L = 20\text{ mH}$, $C = 0.02\text{ F}$, and $R_w = 90\ \Omega$ is **90 Ω**
- x. Another name for a unity gain amplifier is **voltage follower**