

- This is a closed book exam.
- The exam has 5 questions in two pages, answer all of them.
- Good Luck!

1. Find the total current in the load resistor R_L , in Figure 1. Assume the sources are ideal. [10 marks]

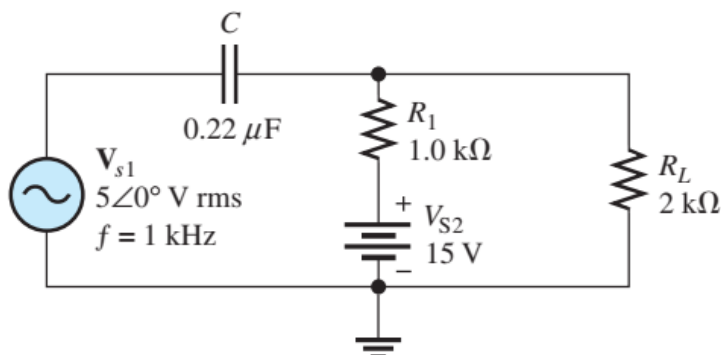


Figure 1

2. Determine the average power generated by each source and the average power absorbed by each passive element in the circuit of Figure 2. [10 marks]

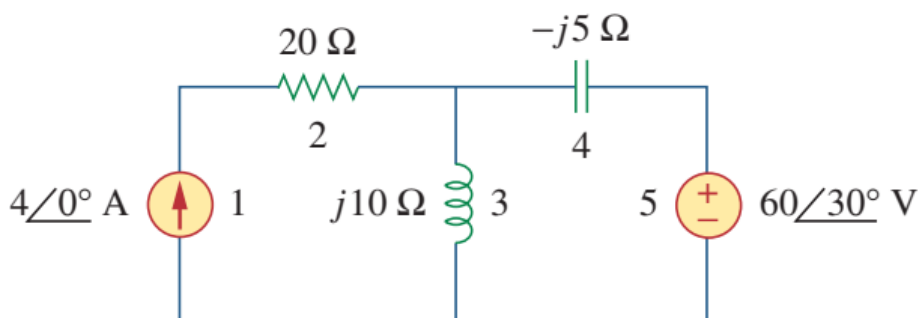


Figure 2

3. Determine $v_o(t)$ for the op amp circuit in Figure 3, if $v_s = 3 \cos 1000t$ V. [10 marks]

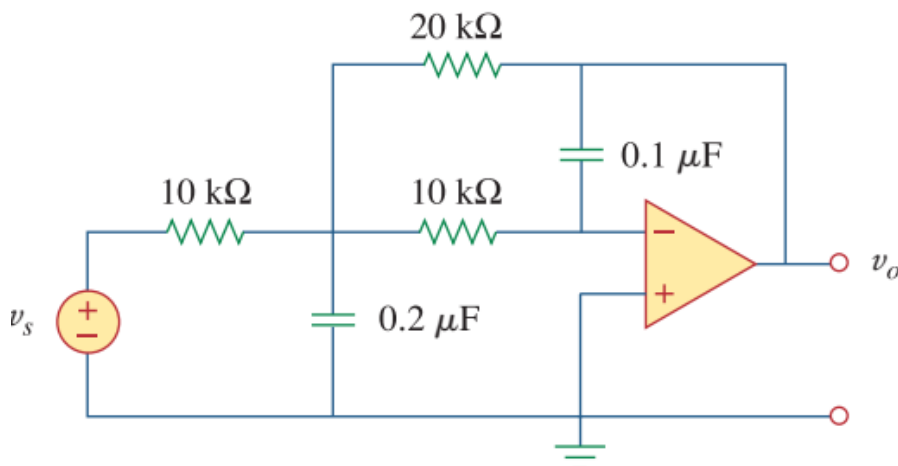


Figure 3

4. Determine the output voltage magnitude at the center frequency (f_0) and the bandwidth for the filter in Figure 4. [10 marks]

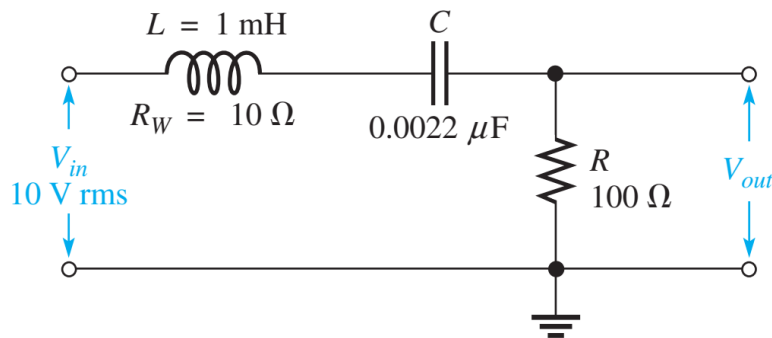


Figure 4

5. Complete the following sentences:

[10 marks]

- i. At the critical frequency, the output of a filter is down from its maximum by
- ii. AC is more easily distributed than DC. This is because
- iii. When the load on an ac source contains only resistance, the current and voltage are
- iv. If a sine wave has a RMS voltage of 12 volts, its Peak-to-Peak voltage will be
- v. The inductive reactance of a 20-mH inductor at a frequency of 60 Hz is
- vi. For a certain load, the true power is 10 W and the reactive power is 10 VAR. The apparent power is
- vii. The filter that can be used to select a signal of one particular radio station is
- viii. The impedance of a capacitor increases with
- ix. An ideal operational amplifier has and
- x. The quality factor (Q) is the ratio of