

Notes:

- Please verify that there are **5** pages in your exam booklet.
- Do all of your answers in the spaces provided in this examination booklet, or on the back side of the page preceding the question.
- Good Luck!

QUESTION (I) (20 points):

- (1.1) State the superposition theorem.
- (1.2) List the steps in applying the theorem.
- (1.3) Describe how you can verify it experimentally.

QUESTION (II) (20 points):

- (2.1) Verify the meters readings in Figure 1 and determine if there is a fault in the circuit.
- (2.2) If R_2 opens, what will meters read?
- (2.3) If the voltage source V_s has an internal resistance $R_s = 100\Omega$, determine its effect on the meters readings.

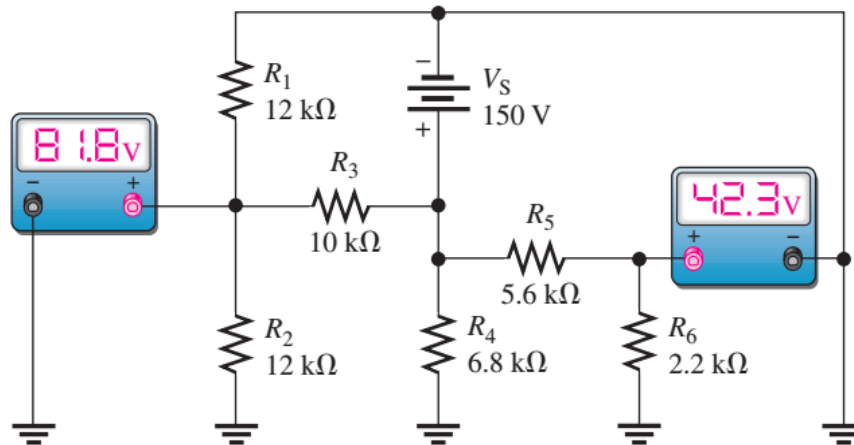


Figure 1

QUESTION (III) (20 points):

- (3.1) What is the resonant frequency and what are the applications of the resonant circuits?
- (3.2) Describe how you can verify the response of a series R-L-C circuit experimentally.
- (3.3) Describe how you can find experimentally Q factor of a coil using a series R-L-C circuit.

QUESTION (IV) (20 points):

Complete the following sentences:

- 1- Two series capacitors (one $1\mu\text{F}$, the other of unknown value) are charged from a 12 V source. The $1\mu\text{F}$ capacitor is charged to 8 V and the other to 4 V. the value of the unknown capacitor is
- 2- The tolerance of a resistor of nominal value $2\text{ k}\Omega$ and a measured resistance of $2020\ \Omega$ is
- 3- the term “Voltage Regulation” means
- 4- In a band-stop filter, the output voltage at the critical frequencies is
- 5- A meter has a scale of 5 percent of FSD on the 10 mA scale. The meter reads 4 mA. the smallest value that the actual current may be is
- 6- Maximum power is transferred from a source to a load when
- 7- The primary purpose of a resistor is to
- 8- A resistor that has the colored bands blue-gray-orange-silver has a minimum value of
- 9- A certain circuit produces 15 V across its open output terminals, and when a load is connected across its output terminals, it produces 12 V. The Thevenin equivalent for this circuit is.....
- 10-For the circuit described in Question 9, maximum power is transferred to
- 11-A sine wave has an average value of 10 V. Its rms value is
- 12-A 10 kHz pulse waveform consists of pulses that are $10\ \mu\text{s}$ wide. Its duty cycle is
- 13-In a four-branch parallel resistor circuit, there are 10 mA of current in each branch. If one of the branches opens, the current in each of the other three branches is
- 14-An ohmmeter is connected across an inductor and the pointer indicates an infinite value. The inductor is
- 15-At the critical frequency, the output of a filter is down from its maximum by
- 16-When the current through a $10\text{ k}\Omega$ resistor is 10 mA, the power is
- 17-In an RC low-pass filter, the output is taken across
- 18-An inductor, a resistor, and a switch are connected in series to a 12 V battery. At the instant the switch is closed, the inductor voltage is
- 19-When the frequency of the source voltage is increased, the impedance of a parallel RC circuit
- 20- One period of a 2 kHz sine wave is found to occupy 5 cm on an oscilloscope screen. The time base must be set at

QUESTION (V) (20 points):

- (5.1) Design and show how to verify experimentally a full wave rectifier circuit.
- (5.2) Briefly discuss the ripple effect on the output from a filtered rectifier circuit.
- (5.3) What is the effect of using the zener diode in rectifier circuits?

With my best wishes,

Prof. Dr. M. Moness